

## ***AN-1317 Selection of External Bootstrap Diode for LM510X Devices***

---

### **ABSTRACT**

This application report discusses the selection of an external bootstrap diode for LM510X devices.

---

### **Contents**

1	Introduction .....	2
2	Theory of Operation .....	3
	2.1 Power Dissipation .....	3
3	Recommended External Bootstrap Diodes .....	5
4	Conclusion .....	5

### **List of Figures**

1	Simplified Schematic of High and Low Side Driver.....	3
2	Gate Driver Power Dissipation (LO + HO) $V_{CC} = 12V$ , Neglecting Diode Losses .....	4
3	Diode Power Dissipation $V_{IN} = 40V$ .....	4
4	Diode Power Dissipation $V_{IN} = 80V$ .....	4

### **List of Tables**

1	Recommended External Bootstrap Diodes .....	5
---	---	---

## 1 Introduction

The gate drive requirements for a power MOSFET utilized as a high side switch, in applications like half-bridge converters or synchronous buck converters can be summarized as follows:

- Gate voltage must be 6 to 12V higher than the source voltage. To fully enhance a high side switch, the gate to source voltage would have to be higher than the threshold voltage plus the minimum necessary voltage to fully enhance the MOSFET.
- The gate voltage must be controllable from the logic level, which are normally referenced to ground. Thus, the control signals need to be level shifted to the source terminal of high side MOSFET (HS node), which in most applications, swings between ground and the high voltage rail.
- The power dissipation of the gate driver must remain within the package thermal limitations.

Highly integrated gate driver IC's integrate following blocks.

- Low side gate driver
- High side level shifter
- High side gate driver
- Under-voltage lockout protection for both high and low side drive
- Bootstrap diode

The bootstrap circuit requires a high voltage and high speed diode along with low ESR/ESL capacitor as shown in [Figure 1](#).

The internal bootstrap diode charges the bootstrap capacitor ( $C_{\text{BOOTSTRAP}}$ ) every cycle when low side MOSFET turns on. The charging of the capacitor involves high peak currents, and therefore transient power dissipation in the internal bootstrap diode may be significant and dependent on the forward voltage drop of the internal diode. The reverse recovery time of the bootstrap diode must be very small, in order to achieve reduction in reverse recovery losses. Both the diode conduction losses and reverse recovery losses contribute to the total losses in the gate driver and need to be considered in calculating the gate driver IC power dissipation.

For high frequency and high capacitive loads, it may be necessary to consider using an external bootstrap diode placed in parallel with internal bootstrap diode to reduce power dissipation. The location of the external bootstrap diode should be very close to the gate driver chip. This application note quantifies the losses in the internal bootstrap diode at various external capacitive loads and supply rail voltages, and the remedies to overcome it.

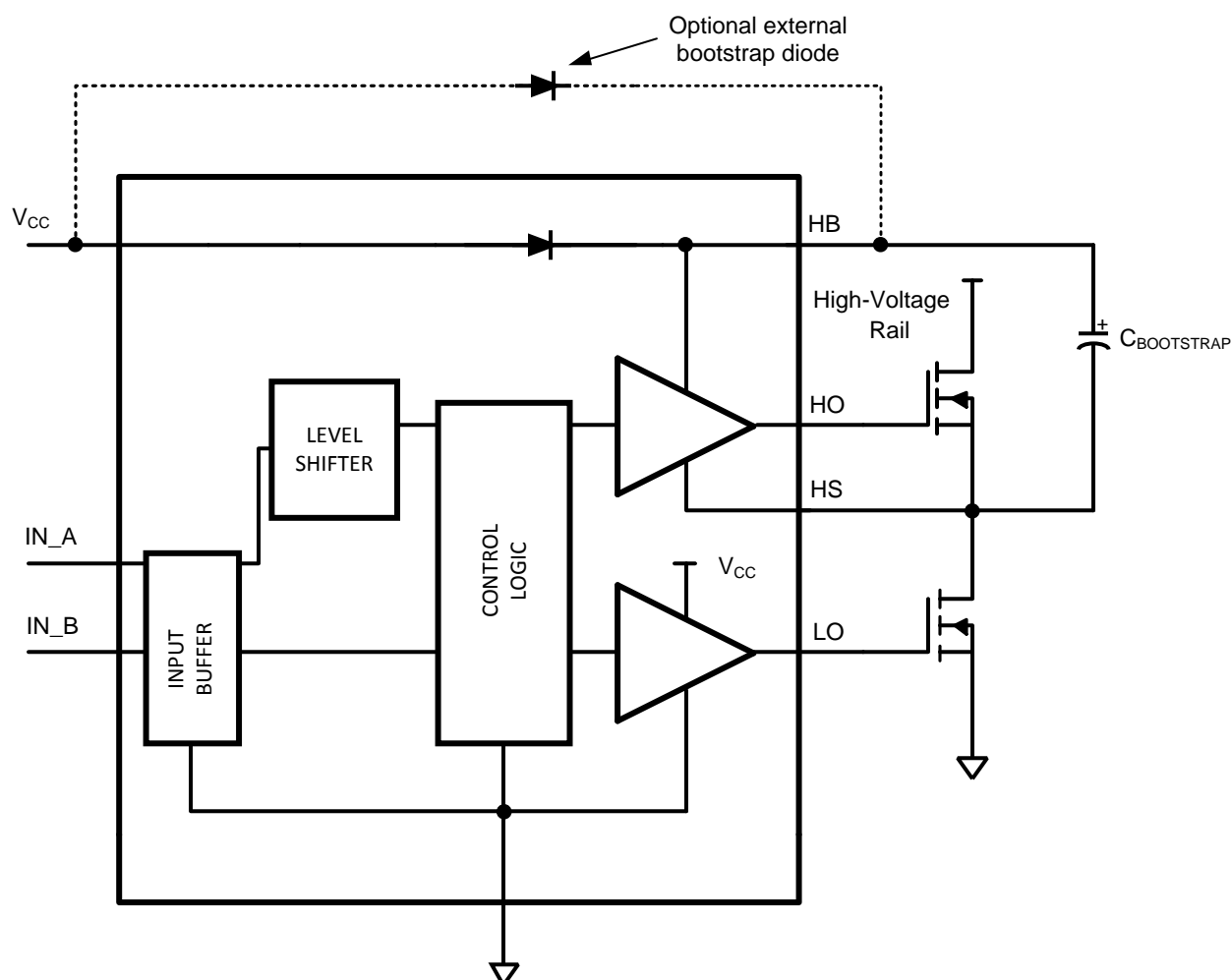


Figure 1. Simplified Schematic of High and Low Side Driver

## 2 Theory of Operation


### 2.1 Power Dissipation

The total IC power dissipation is the sum of the gate driver losses and the bootstrap diode losses. The gate driver losses are related to the switching frequency ( $f$ ), output load capacitance on LO and HO ( $C_L$ ), and supply voltage ( $V_{DD}$ ) and can be roughly calculated as:

$$P_{DGATES} = 2 \times f \times C_L \times V_{DD}^2 = 2 \times f \times Q_g \times V_{DD} \quad (1)$$

Where  $Q_g$  is the total gate charge of the external MOSFET in coulombs.


There are some additional losses in the gate drivers due to the internal CMOS stages used to buffer the LO and HO outputs. Figure 2 shows the measured gate driver power dissipation versus frequency and total gate charge of external MOSFET in coulombs. At higher frequencies and load capacitance values, the power dissipation is dominated by the power losses driving the output loads and agrees with Equation 1. Figure 2 can be used to approximate the power losses due to the LM510X gate drivers. This data was taken by connecting external capacitive loads on both outputs of LM510X driver.

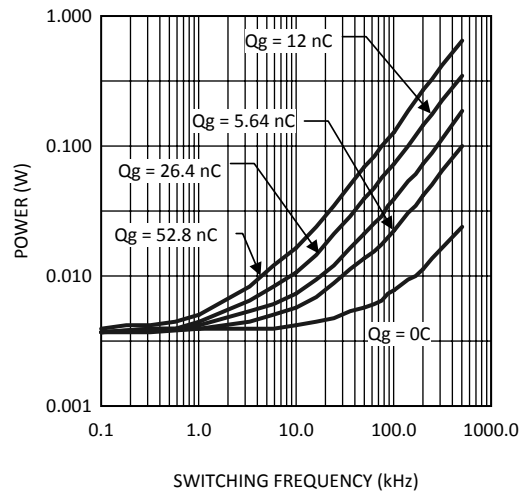


**Figure 2. Gate Driver Power Dissipation (LO + HO)**  
 $V_{CC} = 12V$ , Neglecting Diode Losses

The bootstrap diode power loss is the sum of the forward bias power loss that occurs while charging the bootstrap capacitor and the reverse bias power loss that occurs during reverse recovery. Since each of these events happens once per cycle, the diode power loss is proportional to frequency. Larger capacitive loads require more current to recharge the boot capacitor resulting in more losses. Higher input voltages ( $V_{IN}$ ) to the half bridge result in higher reverse recovery losses. Figure 3 and Figure 4 were generated based on calculations and lab measurements of the diode recovery time and current under several operating conditions. This can be useful for approximating the diode power dissipation.

The total IC power dissipation can be estimated from the plots shown in Figure 2, Figure 3, Figure 4 by summing the gate drive losses with the bootstrap diode losses for the intended application. Because the diode losses can be significant, an external diode placed in parallel with the internal bootstrap diode can be helpful in removing power from the IC. For this to be effective, the external diode must be placed close to the IC to minimize series inductance and have a significantly lower forward voltage drop than the internal diode. (please refer to the LM510X data sheet).

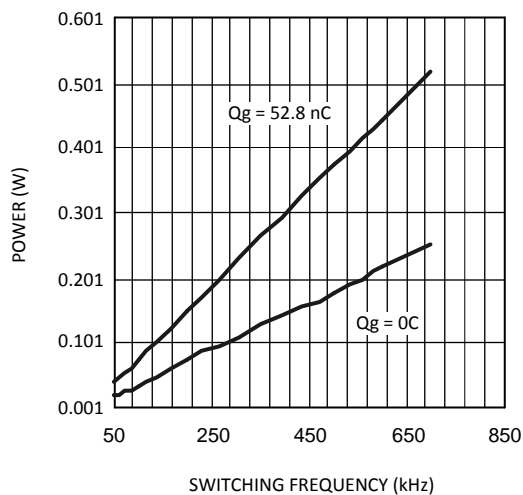

**Figure 3. Diode Power Dissipation**  
 $V_{IN} = 40V$

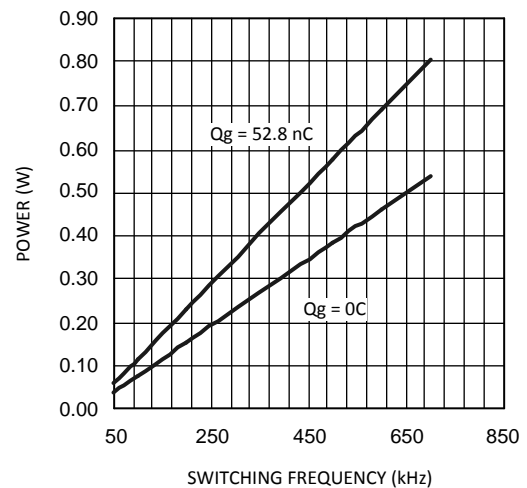

**Figure 4. Diode Power Dissipation**  
 $V_{IN} = 80V$

### 3 Recommended External Bootstrap Diodes

**Table 1. Recommended External Bootstrap Diodes**

Item	Diode Part Number	Manufacturer	Remarks	Approximate Cost/unit
1	CRH01	Toshiba	S-FLATTM PACKAGE	\$0.15
			(3.5mm x 1.6mm)	
2	MURA110T3	ONSEMI	SMA PACKAGE	\$0.11
			(5.5mm x 2.9mm)	
3	BYV40E	PHILIPS SEMI	SOT223 PACKAGE.	-----
			(6.7mm x 6.7mm)	
4	MA2YD1700L	PANASONIC	Schottky diode. High leakage current at high temperatures. Mini2-F1 package.	\$0.18
			(3.5mm x 1.6mm)	

### 4 Conclusion

This application report quantifies the losses in the internal bootstrap diode of LM510X high and low side gate driver. In high frequency and high capacitive load applications, it is sometimes beneficial to use an external bootstrap diode to reduce power dissipated within the IC.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)