
CIOFCO

Check my order Distributor

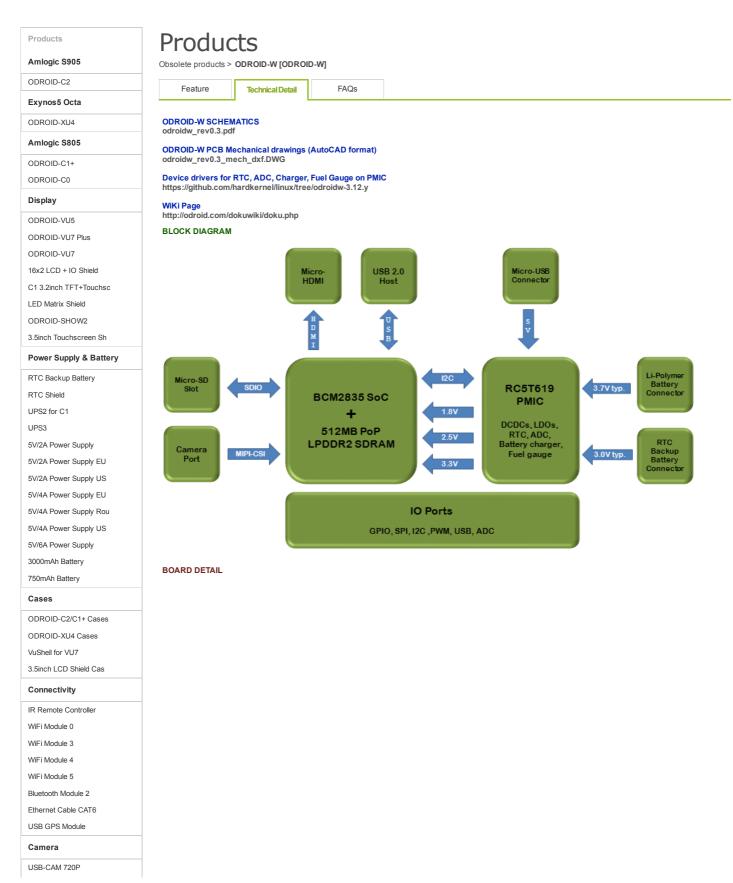Products Wiki Magazine Forum Blog Downloads Store 커뮤니티



oCam : 5MP USB 3.0 Cam
oCam-1MGN-U : Global S
M12 Lens Set : 8/6/3/2
Tripod mount for oCam

Development

C Tinkering Kit

USB-UART Module Kit

Xprotolab Plain

Sound

HiFi Shield 2
HiFi Shield Plus
USB Audio Adapter
USB-SPDIF

Connector

Micro USB-DC Power Bri Connector Pack for ODR 30pin and 12pin Header

Add-on Boards

CloudShell for XU4
Expansion Board
USB IO Board
XU4 Shifter Shield
Universal Motion Joypa
USB3.0 to SATA Bridge
U3 IO Shield

Sensor

myAHRS+ Weather Board 2

U3 Shield Tinkering Ki

Cooler

40x40x25mm Tall Blue H
C1 Heat Sink
Cooling Fan U2
Cooling Fan U3
Cooling Fan X
Cooling Fan X

Cables


HDMI Cable (Micro, Typ
HDMI Cable (Type A-A)
USB3.0 Micro-A to Stan
Micro USB Cable
DC Plug Cable Assembly
DC Plug Cable Assembly
DC Plug Cable Assembly
DC Plug Cable Assembly
USB-DC Plug Cable 2.5m
USB2.0 OTG Cable

HDMI 2.0 Cable (Type A


OS Preinstalled Flash Memory

eMMC Module C2 Linux B
eMMC Module C2 Android
MicroSD C2 Linux
MicroSD C2 Android
eMMC Module XU4 Linux
eMMC Module XU4 Androi
MicroSD XU4 Linux
eMMC Module C1+/C0 Lin
eMMC Module C1+/C0 And

TOP

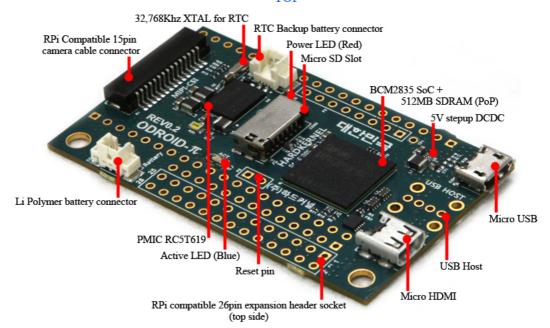

BOTTOM

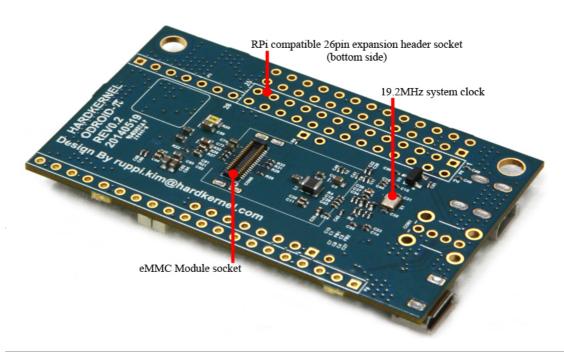

CPU	Broadcom BCM2835 SoC Low Power ARM1176.JZ-F Applications Processor Dual Core VideoCore IV® Multimedia Co-Processor Low power, high performance OpenGL-ES® 1.1/2.0 VideoCore GPU. 1 Gigapixel per second fill rate.
DRAM	Samsung K4P4G324EB Mobile DRAM LPDDR2 4Gb(512MB) PoP 128Mx32bit, 168FBGA package
PMIC	Ricoh RT5T619 Power Management IC It integrates high-efficiency step-down DCDC Converters, low-dropout regulators, Real Time Clock, Li-ion Battery Charger, I2C-Bus Interface, Voltage detections, Thermal shut-down, and 12bit Analog-Digital Converter * Note : ADC input range MUST be 0~2.5 Volt!
Step-up DCDC Converter	TI TPS61259 device provides a power supply solution for battery-powered portable applications. Intended for low-power applications, supports up to 1000-mA load current from a battery discharged as low as 3.4V. The 5 Volt output is used for USB host and HDMI circuitry.
HDMI protector IC	NXP IP4791CZ12 designed to protect mobile HDMI transmitter interfaces. It includes level shifting for the DDC, CEC, hot plug signal ar protection. In addition, all signals are protected by high-level ElectroStatic Discharge (ESD) protection diodes.
Voltage detector IC	Torex XC61FN2412MR for stable system start (Auto-power on) It includes Voltage detector and Delay circuit
Li+ Rechargeable battery connector	Molex 53398-0271 1.25mm pitch Header, Surface Mount, Vertical type (Mate with Molex 51021-0200) Connector for Li-Polymer battery Maximum charging current is limited to 1A. Charging voltage is 4.2V.
RTC battery connector	Molex 53398-0271 1.25mm pitch Header, Surface Mount, Vertical type (Mate with Molex 51021-0200) Connector for RTC backup battery(CR2032 or equivalent)

MicroSD C1+/C0 Linux

MicroSD C1+/C0 Android

eMMC Module Reader

Obsolete products

ODROID

ODROID-7 Full Package

ODROID-A4 Full Package

ODROID-PC Full Package

ODROID-S

ODROID-T

ODROID-VU

ODROID-A Full Package

ODROID-U3

ODROID-U2

ODROID-X2

ODROID-E7 Full Package

ODROID-Q2

ODROID-XU3 Lite

ODROID-XU3

ODROID-XU

ODROID-X

ODROID-XU Lite

ODROID-C1

ODROID-Q

ODROID-XU+E

Smart Power

HiFi Shield for C2/C1+

ODROID-Show

ODROID-UPS

ODUINO One

UPS2 for U3

Weather Board ODROID-W



Copyright 2013 **Hardkernel co., Ltd.** 475-1 ManAnRo, ManAnGu, AnYang, GyeongGi, South Korea ZIP:13962 상호 : (주)하드커널 대표자 : 이제현 I 통신판매업신고번호 : 제 2009-경기안앙-872호 개인정보관리 책임자 : 박화정 사업자등록번호 : 138-81-54116 email : odroid@hardkernel.com Tel : 070-8633-5158/5159/5038 경기도 안양시 만안구 만안로 475-1 우:13962